 


# Power Optimization in FPGA Design of BCD Adder using Clock Gating

FPGA Based System Design – 22EC2020

- ALDRIN G (URK22EC1019)



# BCD ADDER

*Verilog code (BEHAVIOURAL MODELING):*

```
module bcd_adder (  
    input [3:0] a,  
    input [3:0] b,  
    output reg [3:0] sum,  
    output reg cout  
);  
    reg [4:0] temp_sum;  
  
    always @(*)  
    begin  
        temp_sum = a + b;  
  
        if (temp_sum > 4'd9)  
        begin  
            sum = temp_sum + 4'd6;  
            cout = 1;  
        end  
        else  
        begin  
            sum = temp_sum[3:0];  
            cout = 0;  
        end  
    end  
endmodule
```

## **Power Optimized Code using Clock Gating Technique:**

```
module bcd_adder (  
    input [3:0] a,  
    input [3:0] b,  
    output reg [3:0] sum,  
    output reg cout  
);  
    reg [4:0] temp_sum;  
    reg [3:0] prev_a, prev_b;  
  
    always @(*)  
    begin  
        // Check if there is any change in the inputs  
        if (a != prev_a || b != prev_b)  
        begin  
            // Update temporary sum and store previous inputs  
            temp_sum = a + b;  
            prev_a = a;  
            prev_b = b;  
  
            if (temp_sum > 4'd9)  
            begin  
                sum = temp_sum + 4'd6;  
                cout = 1;  
            end  
            else  
            begin  
                sum = temp_sum[3:0];  
                cout = 0;  
            end  
        end  
    end  
endmodule
```

## Key Differences after Design Optimization

**Objective:** Reduce toggling activity in the BCD adder to save power by updating only when inputs change.

### **Modifications:**

1. **Previous State Registers (`prev_a`, `prev_b`):** Store the last state of inputs `a` and `b`.
2. **Condition for Computation:** Add a check in the `always` block to update `temp_sum` only when `a` or `b` changes.

**Result:** This minimizes unnecessary updates, reducing switching activity and saving power by avoiding redundant computations.

## Applying Clock Gating for Power Optimization

1. **Purpose of Clock Gating:** Reduces power consumption by activating logic only when necessary.
2. **Clock Gating Mechanism:** Adds a clock enable signal to control when the logic block executes.
3. **Effect on BCD Adder:** Ensures the BCD adder updates only when there's a change in inputs, reducing unnecessary computations.
4. **Simulation in Combinational Logic:**
  - Since the BCD adder is a combinational block (without a clock signal), we simulate clock gating.
  - Implement a condition to perform addition only if `a` or `b` changes.
5. **Power Savings:** Minimizes toggling activity and power consumption by preventing redundant updates to `temp_sum`.


## Comparison Table:

Power Parameter	Unoptimized Design	Optimized Design	Power Reduction (W)	Percentage Reduction (%)
Total On-Chip Power	2.88 W	0.228 W	2.652 W	92.08%
Dynamic Power	2.801 W	0.157 W	2.644 W	94.39%
Static Power	0.078 W	0.071 W	0.007 W	8.97%


# UNOPTIMIZED BCD ADDER

## Power Report Summary:

Power		Summary   On-Chip
Total On-Chip Power:	2.88 W	
Junction Temperature:	39.4 °C	
Thermal Margin:	45.6 °C (9.1 W)	
Effective $\theta_{JA}$ :	5.0 °C/W	
Power supplied to off-chip devices:	0 W	
Confidence level:	Low	
<a href="#">Implemented Power Report</a>		

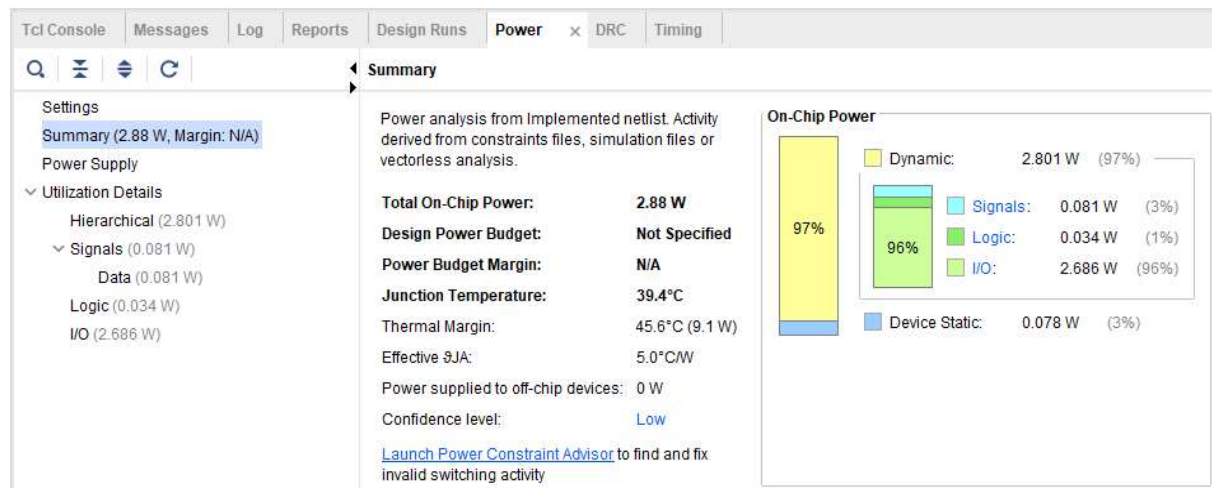


## Schematic:

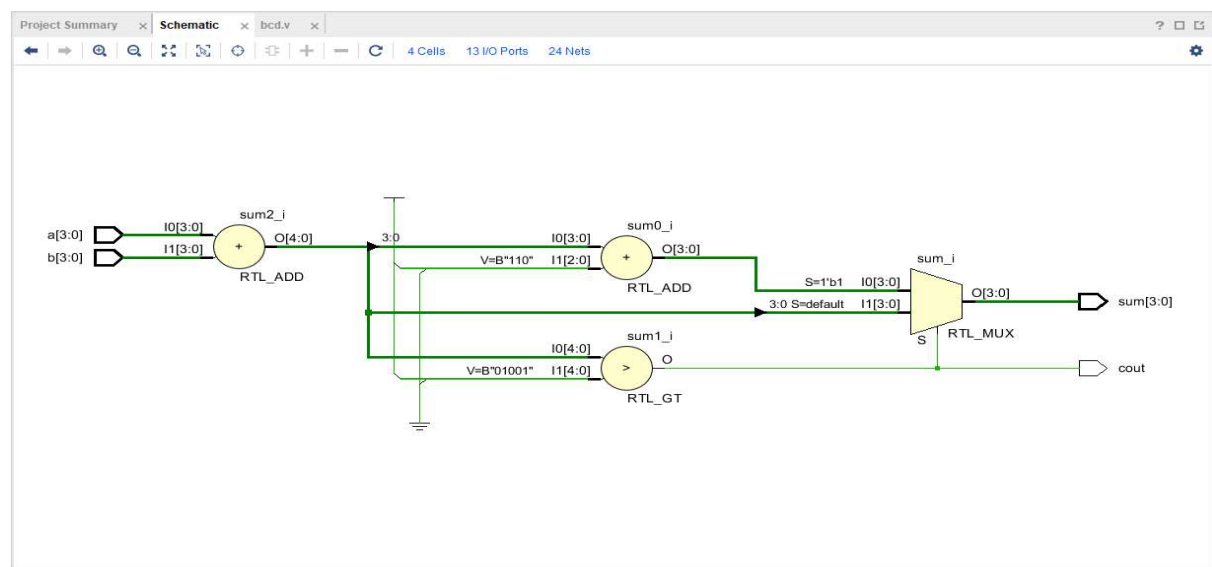

# OPTIMIZED BCD ADDER

## Power Report Summary:

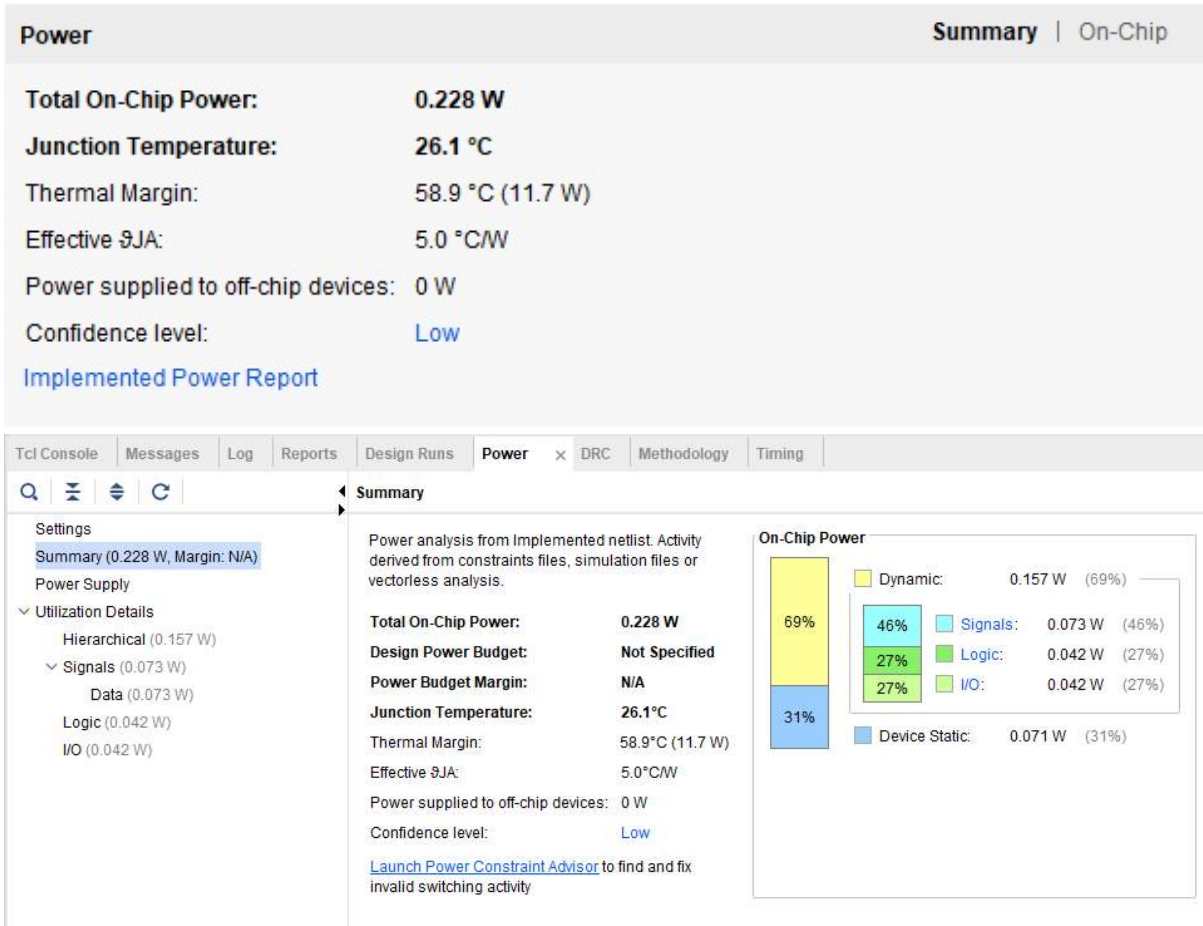

## Schematic:

